

# Contents

## Preface vii

## Chapter 1 Introduction to Electrical Engineering 1

- 1.1 Electrical Engineering 2
- 1.2 Electrical Engineering as a Foundation for the Design of Mechatronic Systems 4
- 1.3 Fundamentals of Engineering Exam Review 12
- 1.4 Brief History of Electrical Engineering 13
- 1.5 System of Units 14
- 1.6 Special Features of This Book 15
  - Virtual Lab 16
  - Find It on the Web! 17
  - CD-ROM Content 17
  - Website 17

## PART I CIRCUITS 18

## Chapter 2 Fundamentals of Electric Circuits 19

- 2.1 Definitions 20
  - Ideal Voltage Sources 20
  - Ideal Current Sources 21
  - Dependent (Controlled) Sources 22
  - Branch 22
  - Node 22
  - Loop 23
  - Mesh 23
  - Network Analysis 24
- 2.2 Charge, Current, and Kirchhoff's Current Law 24
- 2.3 Voltage and Kirchhoff's Voltage Law 30
  - Ground 31
- 2.4 Electric Power and Sign Convention 34
- 2.5 Circuit Elements and Their  $i$ - $v$  Characteristics 38
- 2.6 Resistance and Ohm's Law 39
  - Open and Short Circuits 43
  - Series Resistors and the Voltage Divider Rule 44
  - Parallel Resistors and the Current Divider Rule 47
- 2.7 Practical Voltage and Current Sources 57

- 2.8 Measuring Devices 58
  - The Ohmmeter 58
  - The Ammeter 58
  - The Voltmeter 59
  - Conclusion 60

## Chapter 3 Resistive Network Analysis 73

- 3.1 Network Analysis 74
- 3.2 The Node Voltage Method 75
  - Nodal Analysis with Voltage Sources 82
- 3.3 The Mesh Current Method 85
  - Mesh Analysis with Current Sources 90
- 3.4 Node and Mesh Analysis with Controlled Sources 92
  - Remarks on Node Voltage and Mesh Current Methods 97
- 3.5 The Principle of Superposition 97
- 3.6 One-Port Networks and Equivalent Circuits 100
  - Thévenin and Norton Equivalent Circuits 101
  - Determination of Norton or Thévenin Equivalent Resistance 103
  - Computing the Thévenin Voltage 106
  - Computing the Norton Current 110
  - Source Transformations 112
  - Experimental Determination of Thévenin and Norton Equivalents 115
- 3.7 Maximum Power Transfer 118
- 3.8 Nonlinear Circuit Elements 121
  - Description of Nonlinear Elements 122
  - Graphical (Load-Line) Analysis of Nonlinear Circuits 122
  - Conclusion 126

## Chapter 4 AC Network Analysis 137

- 4.1 Energy-Storage (Dynamic) Circuit Elements 138
  - The Ideal Capacitor 139
  - Energy Storage in Capacitors 145
  - The Ideal Inductor 148
  - Energy Storage in Inductors 154
- 4.2 Time-Dependent Signal Sources 155
  - Why Sinusoids? 157
  - Average and RMS Values 157

- 4.3** Solution of Circuits Containing Energy Storage Elements (Dynamic Circuits) 161  
Forced Response of Circuits Excited by Sinusoidal Sources 162
- 4.4** Phasors Solution of Circuits with Sinusoidal Excitation 163  
Euler's Identity 164  
Phasors 164  
Superposition of AC Signals 167  
Impedance 169  
The Resistor 169  
The Inductor 170  
The Capacitor 171  
Admittance 177
- 4.5** AC Circuit Analysis Methods 179  
AC Equivalent Circuits 183  
Conclusion 190

## Chapter 5 Transient Analysis 201

- 5.1** Transient Analysis 202
- 5.2** Writing Differential Equations for Circuits Containing Inductors and Capacitors 203
- 5.3** DC Steady-State Solution of Circuits Containing Inductors and Capacitors: Initial and Final Conditions 208  
DC Steady-State Solution 208  
Continuity of Inductor Currents and Capacitor Voltages, and Initial Conditions 212
- 5.4** Transient Response of First-Order Circuits 214  
Elements of the Transient Response 214  
General Solution of First-Order Circuits 215  
Natural Response 216  
Forced Response 217  
Complete Response 217  
Energy Storage in Capacitors and Inductors 221
- 5.5** Transient Response of Second-Order Circuits 235  
Deriving the Differential Equations for Second-Order Circuits 235  
Solution of Second-Order Circuits 237  
Elements of the Transient Response 239  
Natural Response of a Second-Order System 239  
Forced Response 243  
Complete Response 244  
Conclusion 258

## Chapter 6 Frequency Response and System Concepts 269

- 6.1** Sinusoidal Frequency Response 270
- 6.2** Fourier Analysis 275  
Computation of Fourier Series Coefficients 277  
Response of Linear Systems to Periodic Inputs 282
- 6.3** Filters 285  
Low-Pass Filters 285  
High-Pass Filters 292  
Bandpass Filters, Resonance, and Quality Factor 295  
Resonance and Bandwidth 296
- 6.4** Bode Plots 308  
Bode Plots of Higher-Order Filters 311  
Conclusion 317

## Chapter 7 AC Power 327

- 7.1** Power in AC Circuits 328  
Instantaneous and Average Power 328  
AC Power Notation 330  
Power Factor 335
- 7.2** Complex Power 335  
Power Factor, Revisited 342
- 7.3** Transformers 355  
The Ideal Transformer 355  
Impedance Reflection and Power Transfer 358
- 7.4** Three-Phase Power 364  
Balanced Wye Loads 368  
Balanced Delta Loads 368
- 7.5** Residential Wiring; Grounding and Safety 372
- 7.6** Generation and Distribution of AC Power 375  
Conclusion 376

## PART II ELECTRONICS 388

## Chapter 8 Operational Amplifiers 389

- 8.1** Ideal Amplifiers 390  
Ideal Amplifier Characteristics 390
- 8.2** The Operational Amplifier 392  
The Open-Loop Model 392  
The Operational Amplifier in Closed-Loop Mode 393

- 8.3** Active Filters 413
- 8.4** Integrator and Differentiator Circuits 418
  - The Ideal Integrator 418
  - The Ideal Differentiator 422
- 8.5** Analog Computers 422
  - Scaling in Analog Computers 425
- 8.6** Physical Limitations of Operational Amplifiers 429
  - Voltage Supply Limits 429
  - Frequency Response Limits 431
  - Input Offset Voltage 435
  - Input Bias Currents 436
  - Output Offset Adjustment 437
  - Slew Rate Limit 437
  - Short-Circuit Output Current 439
  - Common-Mode Rejection Ratio (CMRR) 441
  - Conclusion 446

## Chapter 9 Semiconductors and Diodes 459

- 9.1** Electrical Conduction in Semiconductor Devices 460
- 9.2** The *pn* Junction and the Semiconductor Diode 462
- 9.3** Circuit Models for the Semiconductor Diode 465
  - Large-Signal Diode Models 466
  - Small-Signal Diode Models 474
  - Piecewise Linear Diode Model 480
- 9.4** Rectifier Circuits 483
  - The Full-Wave Rectifier 483
  - The Bridge Rectifier 484
- 9.5** DC Power Supplies, Zener Diodes, and Voltage Regulation 488
- 9.6** Signal Processing Applications 494
  - The Diode Clipper (Limiter) 495
  - The Diode Peak Detector 499
  - The Diode Clamp 499
- 9.7** Photodiodes 503
  - Conclusion 506

## Chapter 10 Bipolar Junction Transistors: Operation, Circuit Models, and Applications 517

- 10.1** Transistors as Amplifiers and Switches 518
- 10.2** Operation of the Bipolar Junction Transistor 520

- Determining the Operating Region of a BJT 523
- Selecting an Operating Point for a BJT 526
- 10.3** BJT Large-Signal Model 534
  - Large-Signal Model of the *npn* BJT 534
- 10.4** BJT Switches and Gates 541
  - Conclusion 545

## Chapter 11 Field-Effect Transistors: Operation, Circuit Models, and Applications 553

- 11.1** Classification of Field-Effect Transistors 554
- 11.2** Overview of Enhancement-Mode MOSFETs 554
  - Operation of the *n*-Channel Enhancement-Mode MOSFET 556
  - Biasing MOSFET Circuits 558
  - Operation of the *p*-Channel Enhancement-Mode MOSFET 562
- 11.3** MOSFET Amplifiers 563
- 11.4** MOSFET Switches 566
  - Digital Switches and Gates 566
  - Analog Switches 571
  - Conclusion 573

## Chapter 12 Power Electronics 577

- 12.1** Classification of Power Electronic Devices 578
- 12.2** Classification of Power Electronic Circuits 579
- 12.3** Voltage Regulators 581
- 12.4** Power Amplifiers and Transistor Switches 584
  - Power Amplifiers 584
  - BJT Switching Characteristics 586
  - Power MOSFETs 587
  - Insulated-Gate Bipolar Transistors 590
- 12.5** Rectifiers and Controlled Rectifiers (AC-DC Converters) 590
  - Three-Phase Rectifiers 593
  - Thyristors and Controlled Rectifiers 594
- 12.6** Electric Motor Drives 600
  - Choppers (DC-DC Converters) 601
  - Inverters (DC-AC Converters) 605
  - Conclusion 608

## Chapter 13 Digital Logic Circuits 613

- 13.1** Analog and Digital Signals 614

- 13.2** The Binary Number System 616
  - Addition and Subtraction 617
  - Multiplication and Division 618
  - Conversion from Decimal to Binary 618
  - Complements and Negative Numbers 619
  - The Hexadecimal System 621
  - Binary Codes 622
- 13.3** Boolean Algebra 625
  - AND and OR Gates 625
  - NAND and NOR Gates 632
  - The XOR (Exclusive OR) Gate 635
- 13.4** Karnaugh Maps and Logic Design 636
  - Sum-of-Products Realizations 639
  - Product-of-Sums Realizations 644
  - Don't Care Conditions 648
- 13.5** Combinational Logic Modules 651
  - Multiplexers 651
  - Read-Only Memory (ROM) 653
  - Decoders and Read and Write Memory 655
  - Gate Arrays and Programmable Logic Devices 656
  - Conclusion 658

## Chapter 14 Digital Systems 665

- 14.1** Sequential Logic Modules 666
  - Latches and Flip-Flops 666
  - Digital Counters 674
  - Registers 681
- 14.2** Sequential Logic Design 683
  - Programmable Logic Controllers 686
- 14.3** Microprocessors 686
- 14.4** Computer System Architecture 689
- 14.5** Microcontrollers 690
  - Computer Architecture 692
  - Number Systems and Number Codes in Digital Computers 693
  - Memory Organization 694
  - Operation of the Central Processing Unit 696
  - Interrupts 697
  - Instruction Set for the MC68HC05 Microcontroller 698
  - Programming and Application Development in a Microcontroller 698
- 14.6** A Typical Automotive Engine Microcontroller 698
  - General Description 698
  - Processor Section 699
  - Memory 701

- Inputs 703
- Outputs 703
- Conclusion 705

## Chapter 15 Electronic Instrumentation and Measurements 709

- 15.1** Measurement Systems and Transducers 710
  - Measurement Systems 710
  - Sensor Classification 711
  - Motion and Dimensional Measurements 711
  - Force, Torque, and Pressure Measurements 712
  - Flow Measurements 713
  - Temperature Measurements 713
- 15.2** Wiring, Grounding, and Noise 716
  - Signal Sources and Measurement System Configurations 716
  - Noise Sources and Coupling Mechanisms 717
  - Noise Reduction 719
- 15.3** Signal Conditioning 720
  - Instrumentation Amplifiers 720
  - Active Filters 725
- 15.4** Analog-to-Digital and Digital-to-Analog Conversion 734
  - Digital-to-Analog Converters 735
  - Analog-to-Digital Converters 740
  - Data Acquisition Systems 746
- 15.5** Comparator and Timing Circuits 750
  - The Op-Amp Comparator 750
  - The Schmitt Trigger 754
  - Multivibrators 758
  - Timer ICs: The NE555 759
- 15.6** Other Instrumentation Integrated Circuits Amplifiers 761
  - DACs and ADCs 762
  - Frequency-to-Voltage, Voltage-to-Frequency Converters, and Phase-Locked Loops 762
  - Other Sensor and Signal Conditioning Circuits 762
- 15.7** Data Transmission in Digital Instruments 767
  - The IEEE 488 Bus 768
  - The RS-232 Standard 771
  - Other Communication Network Standards 775
  - Conclusion 776

**PART III ELECTROMECHANICS 786****Chapter 16 Principles of Electromechanics 787**

- 16.1** Electricity and Magnetism 788
  - The Magnetic Field and Faraday's Law 788
  - Self- and Mutual Inductance 792
  - Ampère's Law 796
- 16.2** Magnetic Circuits 799
- 16.3** Magnetic Materials and  $B$ - $H$  Curves 814
- 16.4** Transformers 816
- 16.5** Electromechanical Energy Conversion 820
  - Forces in Magnetic Structures 821
  - Moving-Iron Transducers 821
  - Moving-Coil Transducers 832
  - Conclusion 841

**Chapter 17 Introduction to Electric Machines 851**

- 17.1** Rotating Electric Machines 852
  - Basic Classification of Electric Machines 852
  - Performance Characteristics of Electric Machines 855
  - Basic Operation of All Rotating Machines 861
  - Magnetic Poles in Electric Machines 862
- 17.2** Direct-Current Machines 864
  - Physical Structure of DC Machines 865
  - Configuration of DC Machines 866
  - DC Machine Models 867
- 17.3** Direct-Current Generators 870
- 17.4** Direct-Current Motors 874
  - Speed-Torque and Dynamic Characteristics of DC Motors 875
  - DC Drives and DC Motor Speed Control 886
- 17.5** AC Machines 887
  - Rotating Magnetic Fields 887
- 17.6** The Alternator (Synchronous Generator) 889

- 17.7** The Synchronous Motor 891
- 17.8** The Induction Motor 896
  - Performance of Induction Motors 903
  - AC Motor Speed and Torque Control 904
  - Adjustable-Frequency Drives 906
  - Conclusion 907

**Chapter 18 Special-Purpose Electric Machines 915**

- 18.1** Brushless DC Motors 916
- 18.2** Stepping Motors 923
- 18.3** Switched Reluctance Motors 931
  - Operating Principles of SR Machine 933
- 18.4** Single-Phase AC Motors 935
  - The Universal Motor 936
  - Single-Phase Induction Motors 939
  - Classification of Single-Phase Induction Motors 944
- 18.5** Motor Selection and Application 949
  - Motor Performance Calculations 950
  - Motor Selection 954
  - Conclusion 955

**Appendix A Linear Algebra and Complex Numbers 961****Appendix B The Laplace Transform 969****Appendix C Fundamentals of Engineering (FE) Examination 979****Appendix D Answers to Selected Problems 993****Index 1007**